

NGSPICE- Usage and Examples

Electronic Devices Lab : Lab 0

Department of Electrical Engineering
Indian Institute of Technology, Bombay
2023-07-31



What is NGSPICE?

- ▶ SPICE is an acronym for **S**imulation **P**rogram with **I**ntegrated **C**ircuit **E**mphasis. First developed at UC Berkeley, it is the origin of most modern simulators.
- ▶ NGSPICE is an open source mixed-signal circuit simulator. It is the result of combining existing SPICE features with some extra analyses, modeling methods and device simulation features.
- ▶ It is freely available for use in Linux and Windows. It is recommended to use Linux for NGSPICE.
- ▶ NGSPICE requires you to describe your circuit as a **netlist**. A netlist is defined as a set of circuit components and their interconnections.



NGSPICE provides you with....

Basic Circuit Elements

- ▶ Passive components- resistors, capacitors, inductors, etc.
- ▶ Sources- independent voltage and current sources, controlled sources

Semiconductor Devices

- ▶ Pre-defined circuit elements such as diodes and transistors
- ▶ Allows you to define or include models of specific devices e.g. specialized transistors and op-amps

Circuit Analysis Techniques

- ▶ DC and AC analyses
- ▶ Transient and Steady-state analyses
- ▶ Pole-Zero, Noise analyses and more




Getting Started with NGSPICE

- ▶ You can use any text editor (gedit or notepad++) to write your circuit netlist. The first line in an NGSPICE file is **not executed**. It is used to describe the aim of the circuit being simulated.
- ▶ All NGSPICE comments start with an asterix, i.e. '*'
- ▶ The NGSPICE file comprises of the circuit netlist followed by the details of the analysis the user wishes to do.
- ▶ NGSPICE files are usually saved with the extension '.cir' or '.spice'.
- ▶ Circuit components are identified by their first letter of naming, called **prefix**, i.e. resistors begin with *r*, capacitors with *c*, bipolar transistors with *q*, MOSFETs with *m*, voltage sources with *v* and so on.
- ▶ All circuit nodes are named/numbered. The netlist requires one ground node (zero potential).



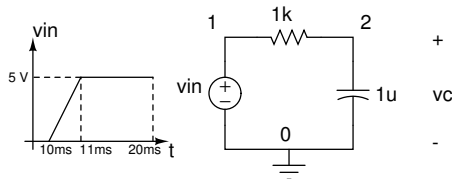Example I- Transient Analysis of an RC Circuit

A simple RC circuit, excited by a user-defined signal V_{in} . We want to find the capacitor voltage i.e. $V_c(t)$. The netlist is as shown.




RC Circuit Transient Response

```
*resistor connected between nodes 1 and 2
r1 1 2 1k
*capacitor connected between nodes 2 and 0
c1 2 0 1u
*piecewise linear input voltage
vin 1 0 pwl (0 0 10ms 0 11ms 5v 20ms 5v)
*transient analysis for 20ms, step size 0.02ms
.tran 0.02ms 20ms
*defining the run-time control functions
.control
run
*plotting input and output voltages
plot v(1) v(2)
.endc
.end
```

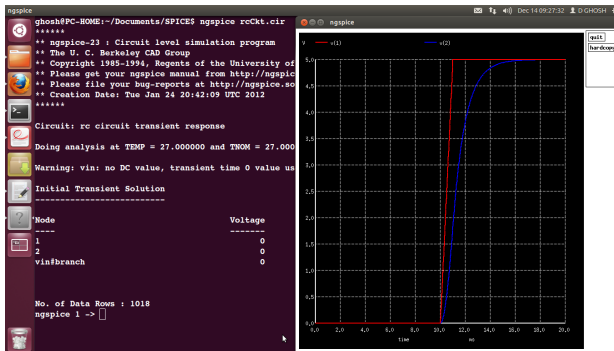Example I- Transient Analysis of an RC Circuit (cont'd)

- ▶ Once you have typed your netlist, save it with an appropriate name, say `rcCkt.cir`.
- ▶ Open the Linux terminal, and change the working directory to the folder where your netlist file is saved. e.g. if the file is in the Documents folder, type `cd ~/Documents` in the the command prompt.
- ▶ Run the netlist file using the command `ngspice rcCkt.cir`
- ▶ And that's it- your netlist should run! A snapshot is as shown.



Inside the NGSPICE Shell

- ▶ Once any netlist is run by NGSPICE, the terminal is hooked to an NGSPICE shell, with a prompt such as `ngspice 1 ->`. You can exit the NGSPICE shell anytime by typing `exit` or `quit`.
- ▶ It is not always necessary to quit NGSPICE every time to run a new netlist. You can use the command `source <filename>.cir` to simulate a new netlist file using the NGSPICE prompt.
- ▶ The commands specified between `.control` and `.endc` in the netlist file may be used in the NGSPICE prompt separately.
- ▶ The waveforms may be saved as a postscript file by clicking on the hardcopy icon on the waveform window. However, this saves it as a default filename in the root directory. A better way to save the waveform in the working directory would be to use the following commands (say for the R-C circuit discussed above)

```
set hcopydevtype=postscript  
hardcopy rcPlot.ps v(1) v(2)
```

- ▶ You can even save the plots using different colours.
Read the NGSPICE manual for that, and much more!



Example II- AC Analysis of RC Circuit

For the same R-C circuit discussed in Example I, let us do the small-signal AC analysis, i.e. find its frequency response. After running this, you should be able to see two plot windows- a magnitude (dB) plot and a phase (degrees) plot.

RC Circuit Frequency Response

```
r1 1 2 1k
```

```
c1 2 0 1u
```

```
*Specifying an AC source with zero dc
```

```
vin 1 0 dc 0 ac 1
```

```
*AC analysis for 1 Hz to 1MHz, 10 points per decade
```

```
.ac dec 10 1 1Meg
```

```
.control
```

```
run
```

```
*Magnitude dB plot for v(2) on log scale
```

```
plot vdb(2) xlog
```

```
*Phase degrees plot for v(2) on log scale
```

```
plot {57.29*vp(2)} xlog
```


```
.endc
```

```
.end
```



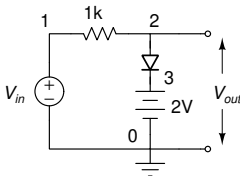Example III- DC Analysis of a Shunt Clipper

A DC analysis involves varying a voltage or a current source output throughout a range of values. Consider the following shunt clipper circuit. We wish to find the V_{out} v/s V_{in} characteristic for this circuit, say for $-5\text{ V} \leq V_{in} \leq +5\text{ V}$.




```
Shunt Clipper DC analysis
r1 1 2 1k
*Specifying a default diode p n
d1 2 3
*Independent DC source of 2V
vdc 3 0 dc 2
*Independent DC source whose voltage is to be varied
vin 1 0 dc 0
*DC Analysis on source vin, to vary from -5 to +5V
.dc vin -5 5 0.01
.control
run
plot v(2) vs v(1)
.endc
.end
```

Use of Subcircuits


- ▶ We have seen how to use electronic devices to build a circuit and test it using NGSPICE.
- ▶ Various electronic devices have their own existing model files that represent the electrical behaviour of that device, which we can use in a netlist. What if we now have an existing circuit, and want to use it to build bigger circuits?
- ▶ A typical example is using an op-amp (operational amplifier) to design a simple amplifier or a filter. Note that, an op-amp is a pre-existing **circuit** and not a device. It is made of many transistors.
- ▶ NGSPICE allows us to define an op-amp as a **subcircuit**. A subcircuit is much like an IC- we know its pins to interface with the outside world, but we need not be familiar with the inside circuit!
- ▶ A subcircuit is a collection of devices familiar to SPICE. A subcircuit is identified by the prefix **x**.
The usage is very similar to that of a model file.

An Example Scenario for Subcircuits

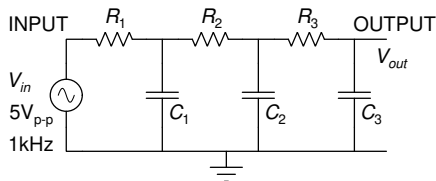Consider the circuit shown (each resistor is $1\text{ k}\Omega$ and each capacitor $1\text{ }\mu\text{F}$)



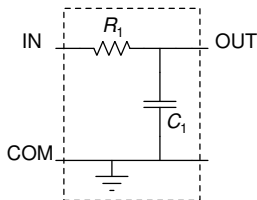- ▶ If we were to write this netlist, there would be a number of useless reiterations of resistors/capacitors.
- ▶ Since the component values are repetitive, we can define each $R - C$ pair as a subcircuit, with terminals IN, OUT and COM.



Multiple R - C Networks using Subcircuits

The netlist to do a transient analysis for the above circuit is as follows

RC Circuit Transient Analysis using Subcircuits

```
*Defining the Subcircuit RC_subcircuit:  <name> <pin1> <pin2> <pin3>
.subckt RC_subcircuit IN OUT COM
r IN OUT 1K
c OUT com 1u
.ends

*Subcircuit definition ends here
vsin INPUT gnd sin(0 2.5 1K 0 0)

*Invoking RC subcircuit with an 'x'
xrc1 INPUT 1 gnd RC_subcircuit
xrc2 1 2 gnd RC_subcircuit
xrc3 2 OUTPUT gnd RC_subcircuit

.control
tran 0.02m 40m
plot v(INPUT)
plot v(OUTPUT)
.endc
.end
```

Multiple R-C Networks using Subcircuits (cont'd..)

In continuation, a subcircuit can be invoked, and different component values can be assigned while invoking (similar to parameter passing). Let us see how!

RC Circuit Transient Analysis using Subcircuits

*Providing some default component values

```
.subckt RC_subcircuit IN OUT COM r1 = 1k c1 = 1u
```

```
r IN OUT {r1}
```

```
c OUT COM {c1}
```

```
.ends
```

```
vsin INPUT gnd sin(0 2.5 1k 0 0)
```

```
xrc1 INPUT 1 gnd RC_subcircuit
```

*Instantiating component values for 2nd subcircuit

```
xrc2 1 2 gnd RC_subcircuit r1 = 100 c1 = 0.1u
```

```
xrc3 2 OUTPUT gnd RC_subcircuit
```

```
.control
```

```
tran 0.02m 40m
```

```
plot v(INPUT) v(OUTPUT)
```


```
.endc
```

```
.end
```

The quantities in {} are parameters, treated as mathematical quantities. Apart from xrc2, all other subcircuits have the default r1 and c1 values.



Example- Integrator using op-amp (741)

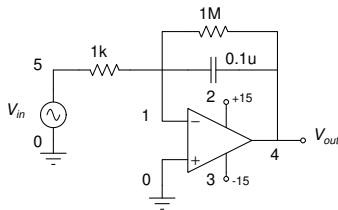

Integrator using op-amp 741

*Including the predefined op-amp subcircuit file

.include ua741.txt

*Connections as mentioned in subcircuit file

x1 0 1 2 3 4 UA741

r1 5 1 1k

c1 4 1 0.1u

rf 4 1 1Meg

vcc 2 0 dc 15v

vee 3 0 dc -15v

*Giving a sinusoidal input

vin 5 0 sin (0 1v 1k 0 0)

.tran 0.02ms 6ms

.control

run

plot v(5) v(4)

.endc

.end

- ▶ Consider the shunt clipper shown in Example III. Change (a) the diode connections (b) the 2 V battery polarity and simulate to observe V_{out} v/s V_{in} variation. For each case, give a 1 kHz sinusoidal input and observe the output waveform (six cycles).
- ▶ Write an NGSPICE netlist for a diode-based bridge rectifier and simulate it to observe the rectified voltage across a load resistor, by giving a 12 V, 50 Hz input. Also, observe the V_{out} v/s V_{in} transfer characteristics.